 


Carry-Skip-Adder

- consider addition of the following numbers

$$\dots a_{k+2} a_{k+1} a_k 010101 a_{l+2} a_{l+1} a_l \dots$$


$$\dots b_{k+2} b_{k+1} b_k 101010 b_{l+2} b_{l+1} b_l \dots$$
- if $c_{l+3} = 1 \rightarrow$ carry will propagate to position k
- to speed-up operation, propagation is skipped to position i without waiting for rippling
- operation time varies according to operands as in carry-complete addition
- to implement carry-skip adder, stages are divided into blocks




- carry-skip logic is added to each block to detect when carry-in the block can be passed directly to the next block
- define carry transfer $T_i = a_i + b_i$
- carry skipping can be detected for a block size of m as follows (carry propagates through all stages):

$$T_j \cdot T_{j+1} \dots T_{j+m-1} = 1 \quad (= (a_j + b_j) \cdot (a_{j+1} + b_{j+1}) \dots)$$
- note: this takes into account both propagated and generated carries!
- carry out from the block (m -bits in a block) is
 
$$\underbrace{T_j \cdot T_{j+1} \dots T_{j+m-1} \cdot c_j}_{skipped} + \underbrace{c_{j+m}}_{generated}$$



 - block size in carry-skip adder is very important
- worst case operation time takes place when
 - carry is generated in the first block
 - carry skips intermediate stages
 - carry is killed in the last block



- worst case addition time is $\left(\frac{2n}{m} + 4m - 4\right) \tau$ (n =adder width, m =block size)

- for optimal block size, minimize delay:

$$\frac{d}{dm} \left(\frac{2n}{m} + 4m - 4 \right) = -2 \left(\frac{n}{m^2} - 2 \right) \equiv \\ \Rightarrow m = \sqrt{\frac{n}{2}}$$

- in practise, non-uniform block sizes gives the best performance
- in general, outer blocks should be smaller than middle blocks